

# **Electronic design with evolutionary algorithms**

Adrian Thompson et al. (University of Sussex, UK)

Review by Alain Girault

# The idea

To use **evolutionary algorithms** in order to design electronic circuits

⇒ sometimes known as "genetic algorithms"

In order to obtain circuits with an **emergent behaviour**

**Emergent** = behaviour that cannot be predicted in detail given only the knowledge of the individual components and connections

⇒ **too complex** for a human brain to understand!

# The experiments

Try to design a **robust** electronic circuit for **tone detection**

Use Xilinx **FPGA** XC6216 circuits

Size used =  $10 \times 10$  cells only, i.e., 100 cells (out of  $64 \times 64$ )

Use 4 different circuits under 4 different temperature conditions

⇒ hence **robustness**

# Specifications of the tone detector

**input** = square wave either 1kHz or 10kHz

**output** = 0 or 1 depending on the input

# Specifications of the tone detector

**input** = square wave either 1kHz or 10kHz

**output** = 0 or 1 depending on the input

**Easy** to design with conventional method

But you would get a **much bigger** circuit

# The evolution strategy

A (1+1) Evolution Strategy [Schwefel & Rudolph 1995]

A mutation selects one of the FPGA's 100 cells at random,  
selects one of that cell's 10 muxes at random,  
reconfigures it to select a different input at random

This mutation is applied **three times** to produce each offspring

# Fitness function

$F$  is used to select the **best offspring** at each generation

$c$  is the FPGA chip number  $\in [1, 4]$

$S_1/S_{10}$  is the set of 1kHz/10kHz tone tests

$t$  is the tone test number  $\in S_1 \cup S_{10}$  and  $T = |S_1 \cup S_{10}|$

The output of  $c$  is fed to an analogue integrator giving a value  $i_t^c$  proportional to the average output voltage of  $c$  over the test  $t$

$$E^c = \frac{1}{2T} \left| \sum_{t \in S_1} i_t^c - \sum_{t \in S_{10}} i_t^c \right| \quad \text{and} \quad F = \min_{c=1}^4 (E^c)$$

# The algorithm

Download the initial parent configuration to the FPGAs

Measure  $F_{parent}$  over 50 tone tests

**repeat**

    Generate three mutations to update all FPGAs

    Measure  $F_{offspring}$  over 24 tone tests

**if**  $F_{offspring} \geq F_{parent}$  **then**

        The offspring becomes the new parent

**else**

        Revert the three mutations

**end if**

**if** 15 offspring have failed to replace their parent **then**

        Reset all the FPGAs and reconfigure them from the parent

**end if**

**until** user decides



# Choice of Adam/Eve

Generate circuits at random until one is found to have an **above average** fitness test:


⇒ 75679 individuals were generated at random

⇒  $F_{Adam/Eve} = 0.43$


25000 triple-mutations out of 861348 attempted

⇒  $F_{final} = 6.17$

# Functional part






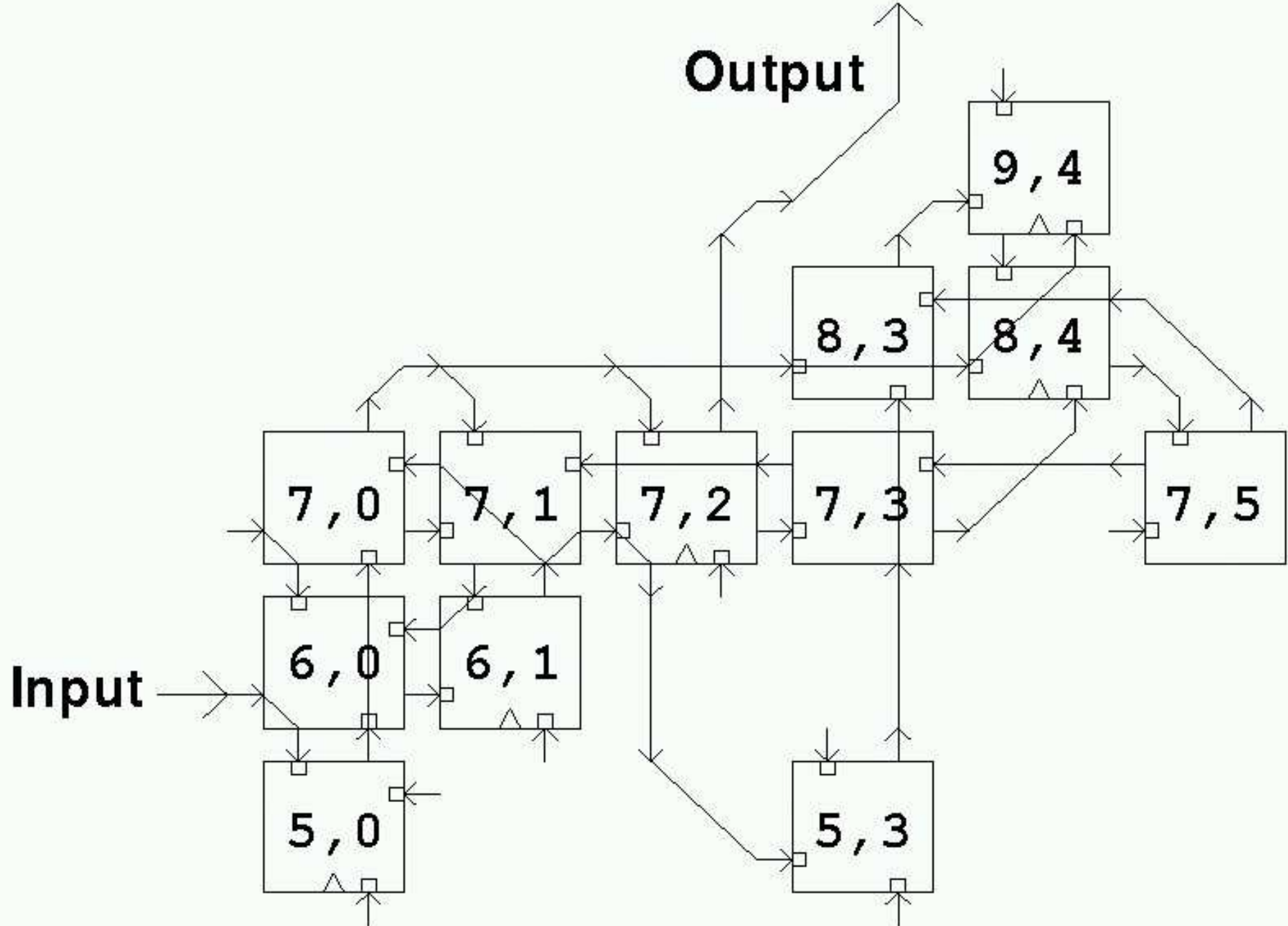


# Left part

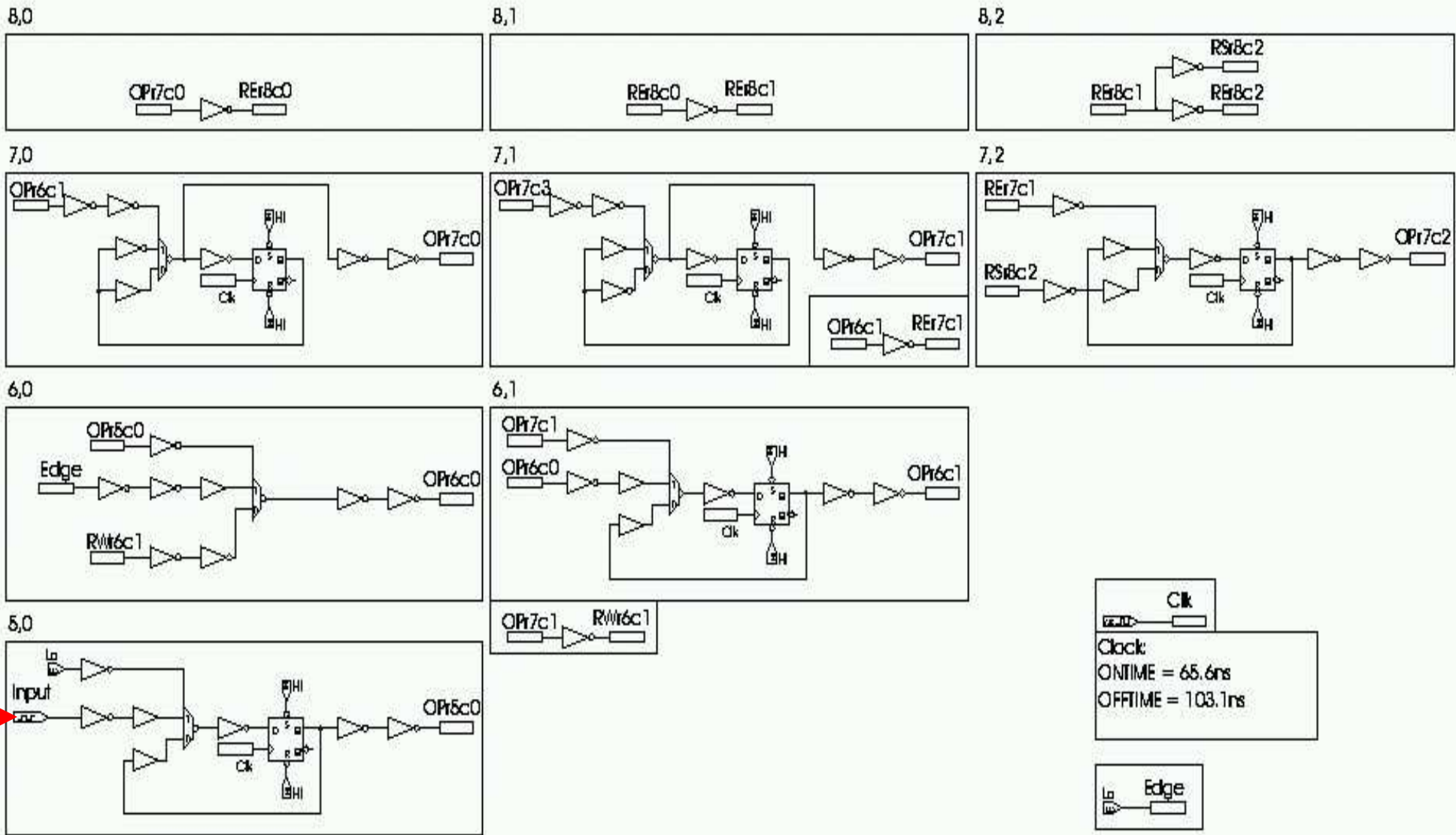


INPUT

# Right part

      

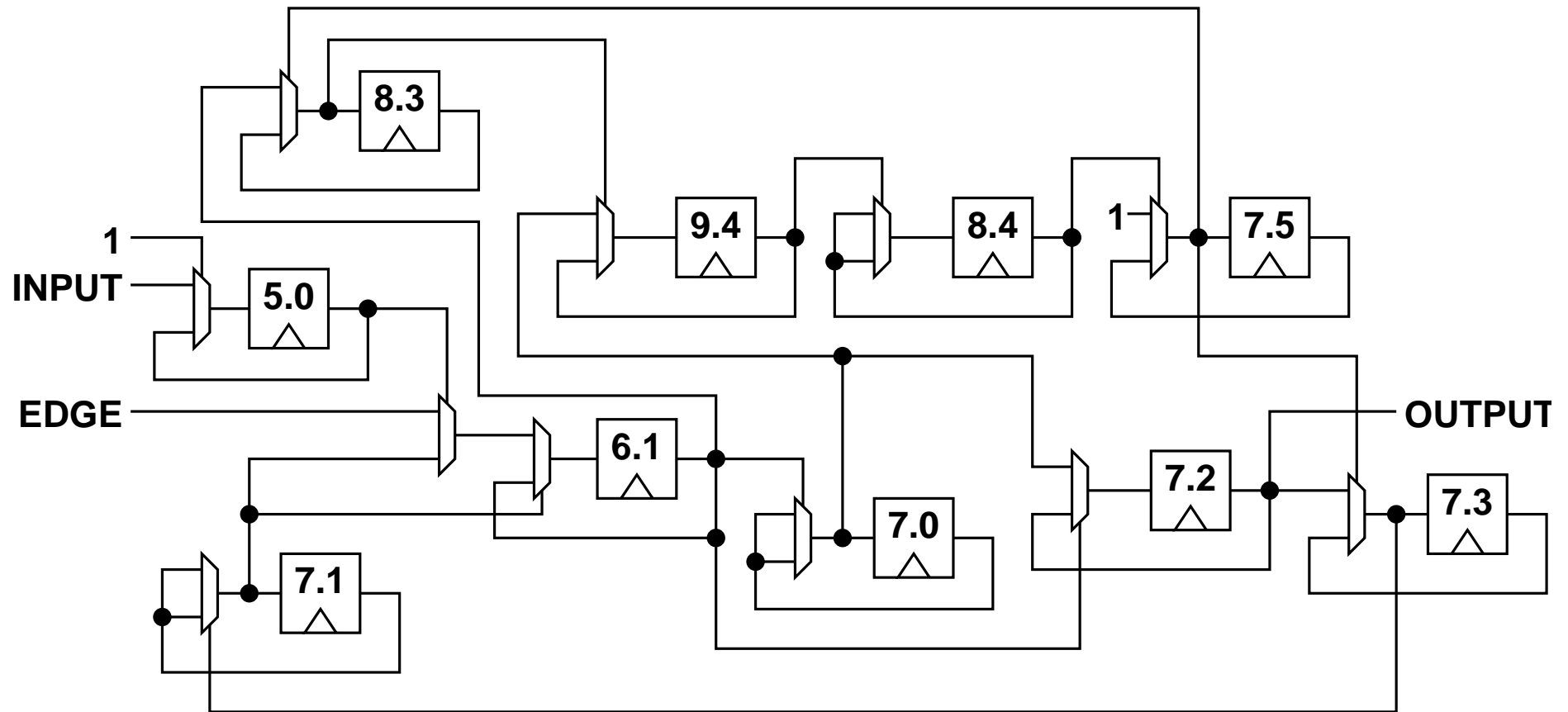
# A lot of nested loops


101 basic gates (inverters), 12 muxes, 10 latches (D flip-flop)



# Core mechanism

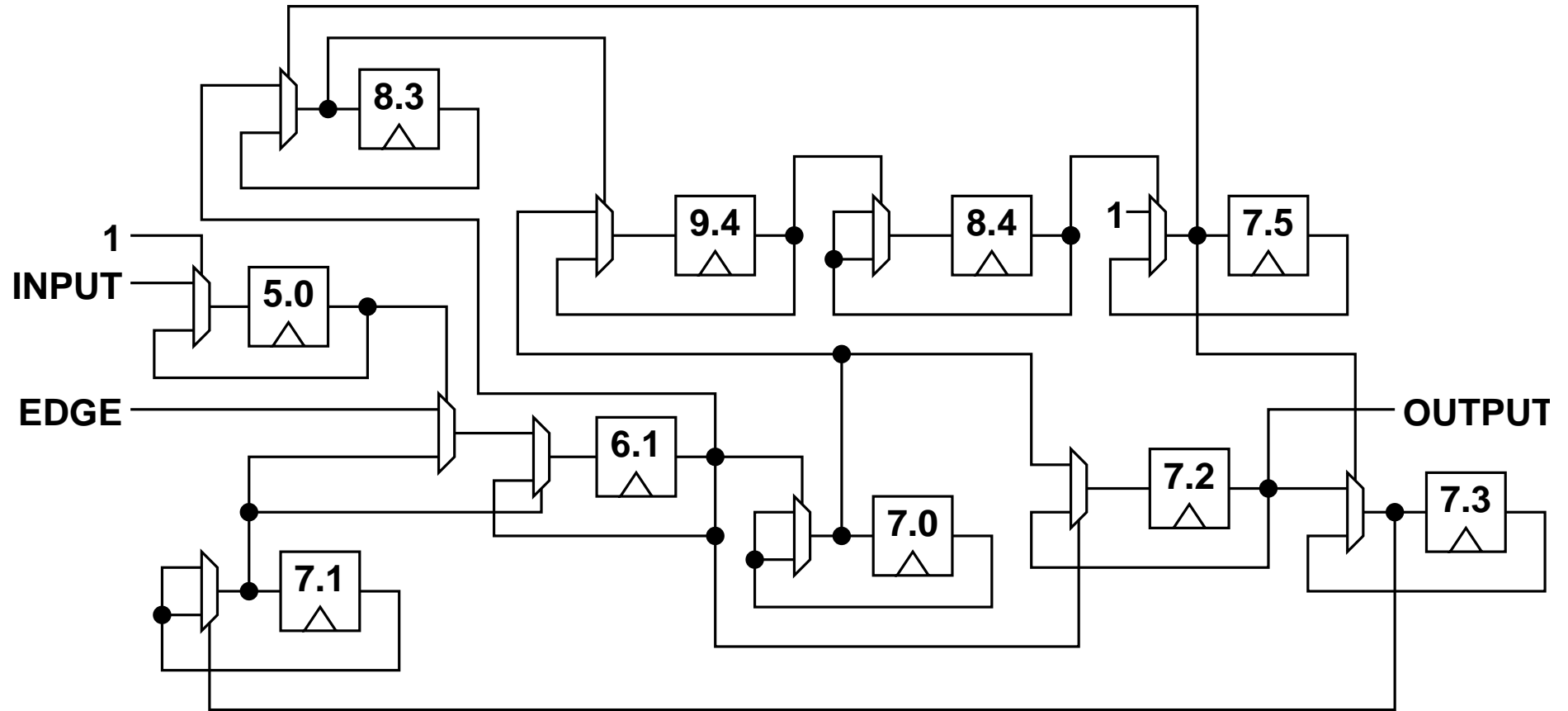


# Core mechanism

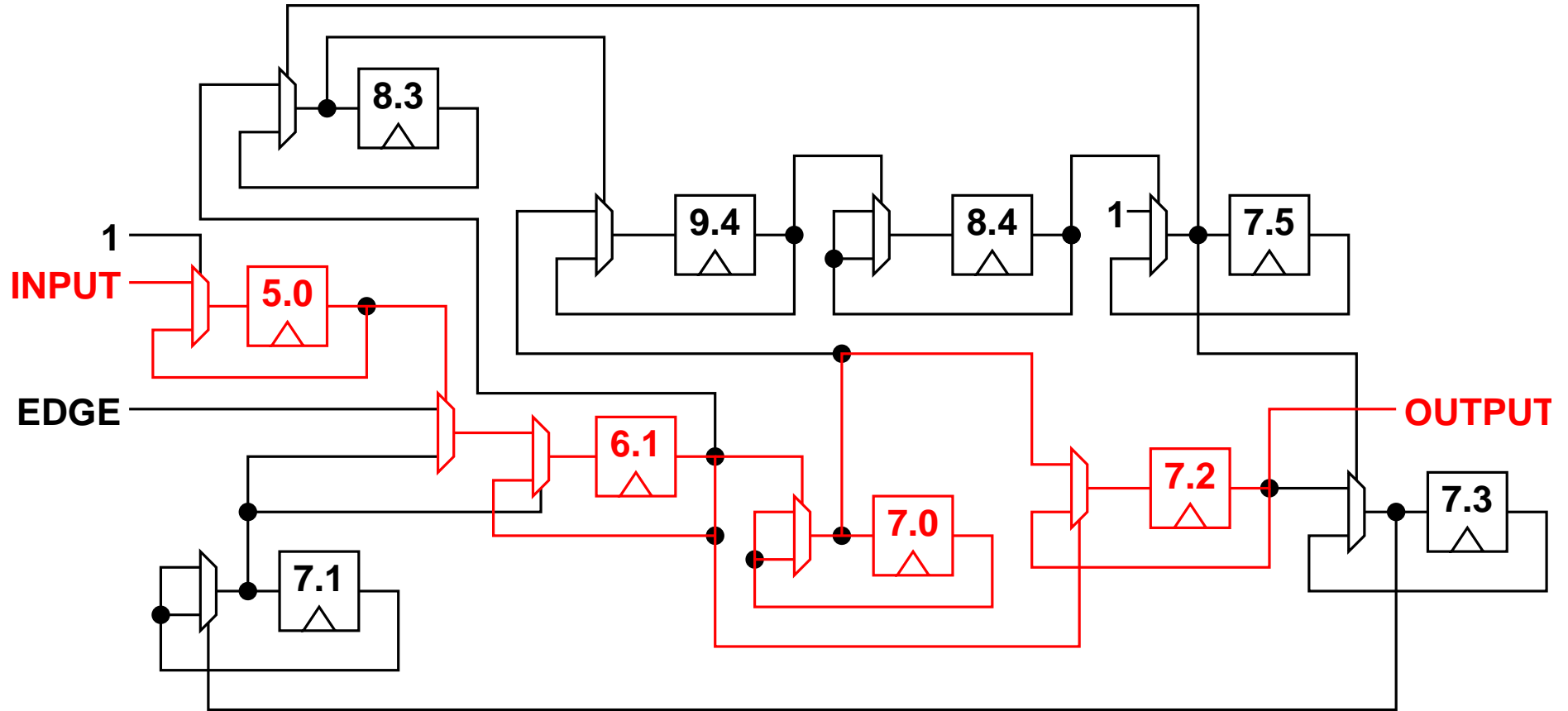

Only four cells are used: (5,0), (6,1), (7,0), and (7,2)


# Core mechanism

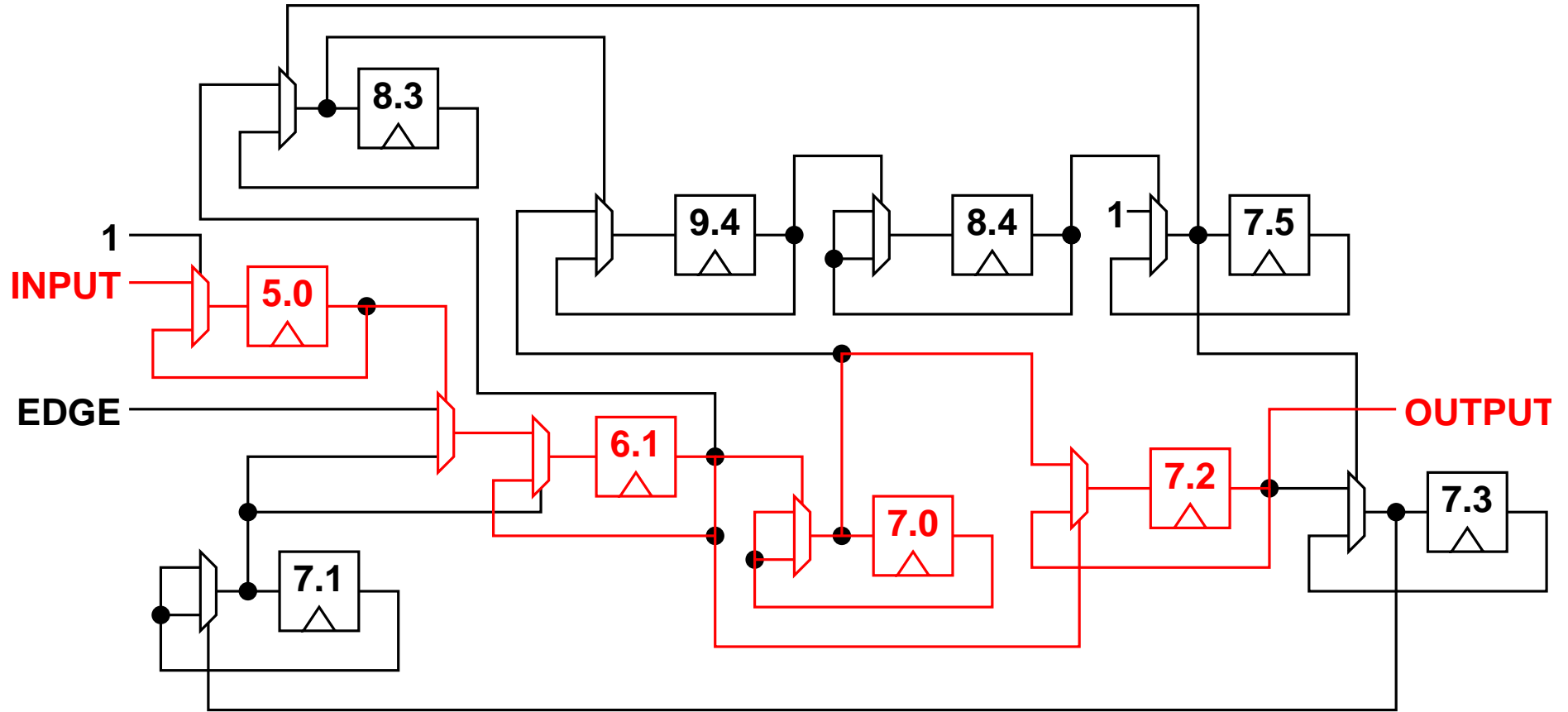

The input is first **retimed** in cell (5,0) to 6kHz




# Core mechanism

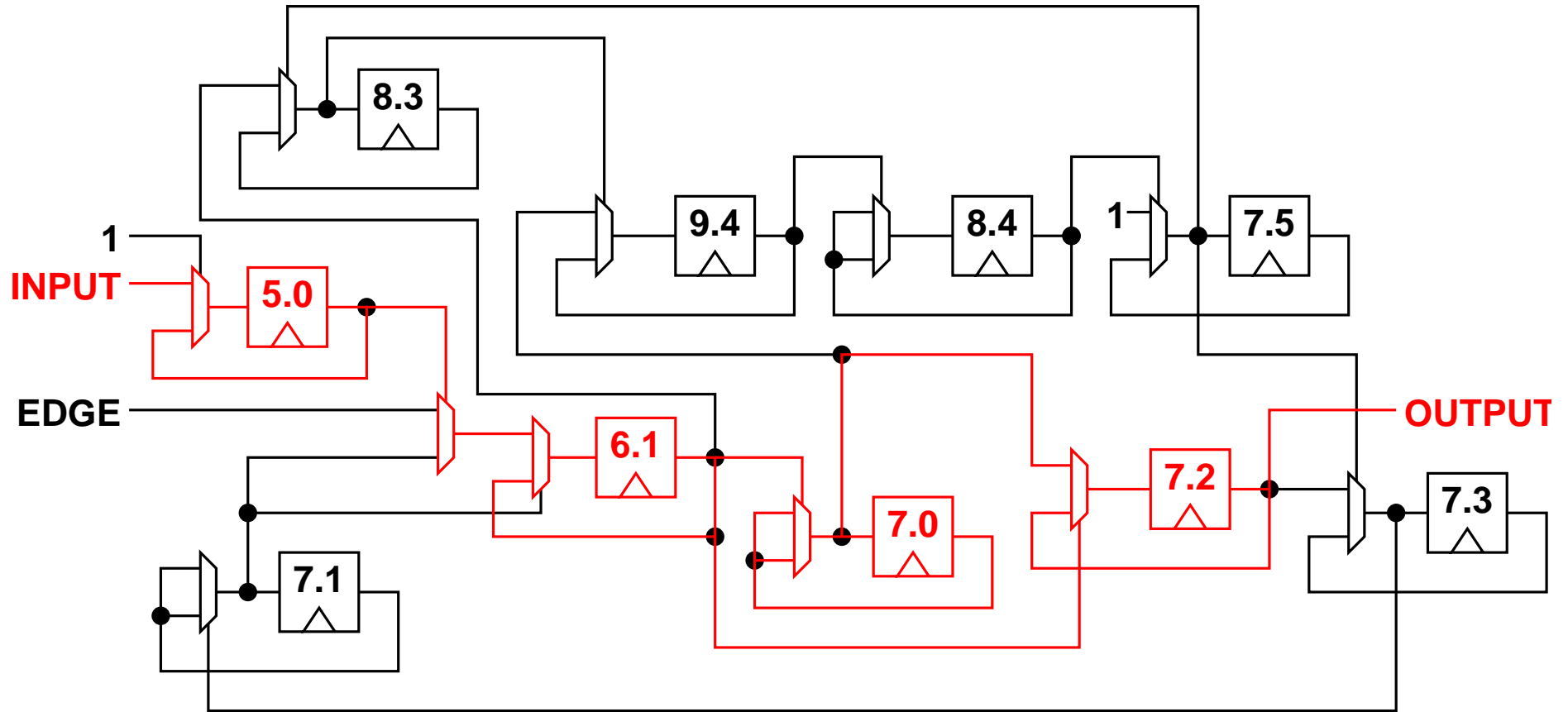


When the retimed input is **high**, cell (7,0) **toggles** at the clock frequency

# Core mechanism

 


When the retimed input is **low**, this oscillation **stops**

# Core mechanism

 


The **number of times** the oscillator toggles is completely determined by how long the raw input is high, and hence the **input frequency**

# Core mechanism

 

Finally, cell (7,2) holds the final value of the previous oscillation while the next one is going on

# Global mechanism

 


This core mechanism with cells (5,0), (6,1), (7,0), and (7,2) produces a **constant output** for one input frequency, and a **toggling output** for the other input frequency

The other cells in the circuit serve to **delay** the retimed input

This delay is **constant** for falling edges, but **variable** for rising edges, function of the current circuit output

# Global mechanism

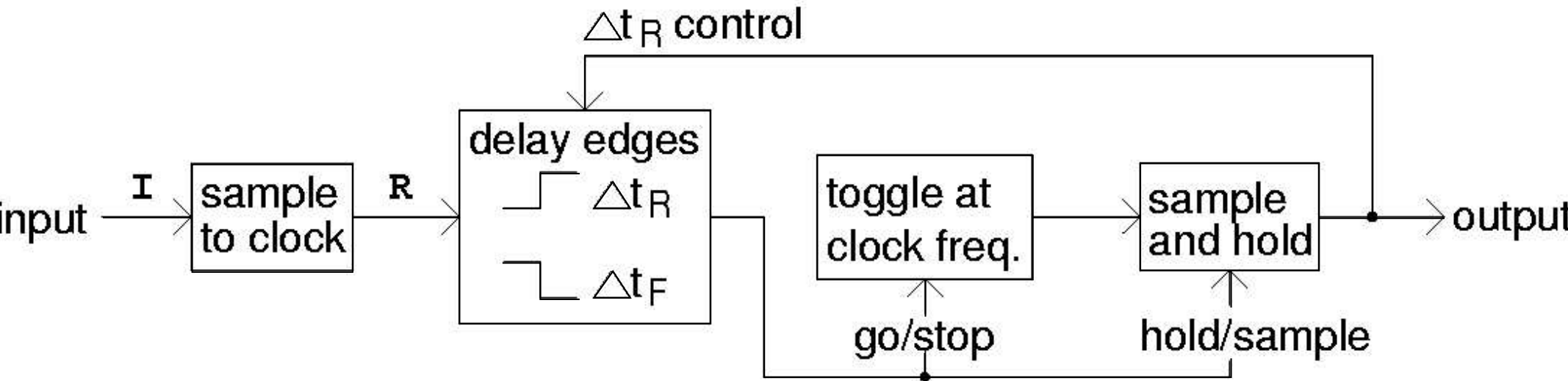

If the input is 1kHz while the output is high (or 10kHz/low),  
**odd toggling** in a high half cycle of the input  
⇒ the output will **change state**

If the input is 1kHz while the output is low (or 10kHz/high),  
**even toggling** in a high half cycle of the input  
⇒ the output will **remain constant**

"The implementation of the variable delay is not yet understood"

# Results and conclusion

The final circuit works **perfectly** from  $-27^{\circ}$  to  $60^{\circ}$

When the input changes, the output changes **after several cycles**

Due to the stabilisation of the cycles involving latches

This digital circuit uses **analogue time delays**, which are **avoided** in digital design!

**The evolution strategy does not care about design rules!**